

## Solutions Manual

# Power Electronics: Converters, Applications and Design

## SECOND EDITION

**Ned Mohan**

Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota 55455

**Tore M. Undeland**

Department of Electrical Engineering  
and Computer Science  
Norwegian Institute of Technology  
N-7034, Trondheim, Norway

**William P. Robbins**

Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota 55455

### Problem 3-5

(a) This is illustrated for only the waveform in Prob 3-3(a).

$$(i) F_1 = \frac{1}{\sqrt{2}} \frac{4}{\pi} A = 0.9 A$$

$$F_{rms} = A$$

$$\therefore \frac{F_1}{F_{rms}} = \frac{1}{\sqrt{2}} \frac{4}{\pi} = 0.9$$

$$(ii) F_{dis} = \sqrt{F_{rms}^2 - F_1^2} = 0.436 A \text{ using Eq 3-35}$$

$$\therefore \frac{F_{dis}}{F_{rms}} = 0.436$$

(b) This is illustrated only for the waveform in Prob 3-3(f).

$$F_0 = \frac{20}{\pi} \text{ [from Prob 3-3 f solution]}$$


$$F_{rms} = 7.071 \text{ [from Prob 3-4 solution]}$$

$$\therefore \frac{F_0}{F_{rms}} = 0.9$$

The same procedure can be used for the rest of the waveforms.
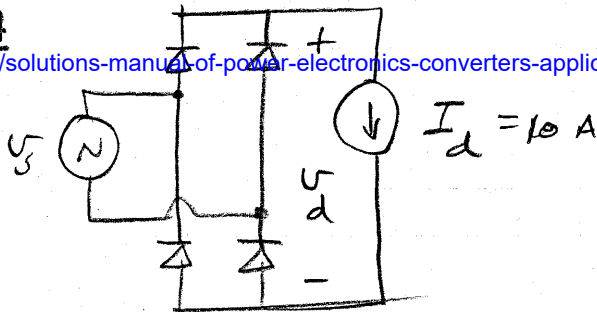
### Problem 5-4

<https://buklibry.com/download/solutions-manual-of-power-electronics-converters-applications-and-design-by-mohan-undeland-2nd-edition/>



(a)  $V_s$ : sinusoidal,  $V_s = 120 \text{ V}$   $\therefore V_d = 0.9 V_s = 108 \text{ V}$

$$P_d = V_d I_d = 1080 \text{ W.}$$

$$A_u = 200 u = 2 \omega L_s I_d$$

$$\therefore u = \frac{2 \omega L_s I_d}{200} \text{ rad} = 0.0377 \text{ rad} = 2.16 \text{ deg}$$




$$V_{do} = 200 \text{ V}$$

$$V_d = V_{do} - \frac{A_u}{\pi} = 200 - \frac{2 \omega L_s I_d}{\pi} = 197.6$$

$$P_d = V_d I_d = 1976 \text{ W}$$

$$\text{drop } \Delta V_d \% = \frac{V_{do} - V_d}{V_{do}} \times 100 = 1.2 \%$$

(b)

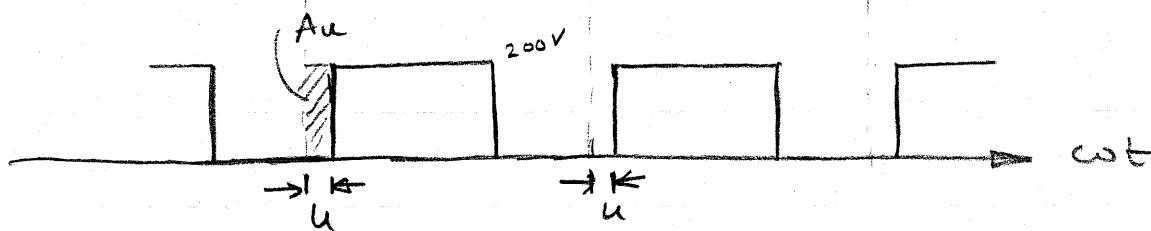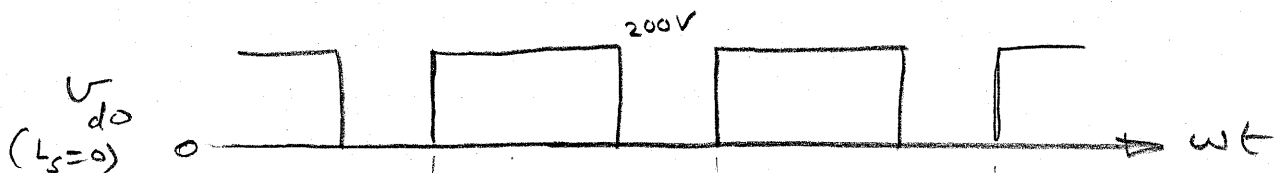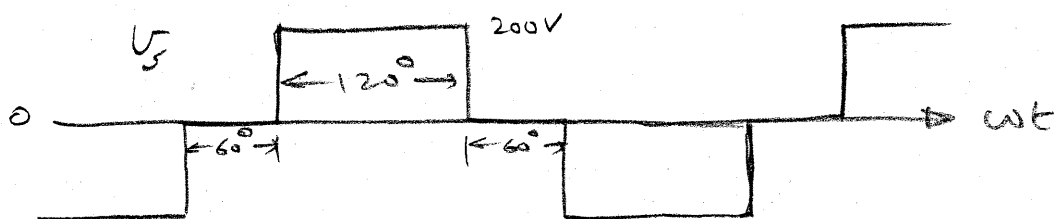

$$V_{do} = 200 \times \frac{120}{180} = 133.33 \text{ V}$$

$$A_u = 200 u = 2 \omega L_s I_d$$

$$u = \frac{2 \omega L_s I_d}{200} \text{ rad} = 0.0377 \text{ rad} = 2.16 \text{ deg}$$

$$V_d = V_{do} - \frac{A_u}{\pi} = 133.33 - \frac{2 \omega L_s I_d}{\pi} = 130.93 \text{ V}$$

$$P_d = V_d I_d = 1309.3 \text{ W}$$

$$\text{drop } \Delta V_d \% = 1.8 \%$$

$$-\frac{\pi}{6} < \theta < \frac{\pi}{6}$$


Calculate  $I_d$ :

$$\begin{aligned} I_d &= \frac{\int_{-\pi/6}^{\pi/6} i_d(\theta) d\theta}{\frac{\pi}{3}} \\ &= \frac{3}{\pi} \frac{V_{LL}}{\omega L_d} \int_{-\pi/6}^{\pi/6} (\sqrt{2} \sin \theta - 1.35\theta + 0.0129\theta^2) d\theta \\ &= \frac{3V_{LL}}{\pi\omega L_d} \left[ -\sqrt{2} \cos \theta - \frac{1.35}{2} \theta^2 + 0.0129\theta^3 \right]_{-\pi/6}^{\pi/6} \\ &= \frac{3V_{LL}}{\pi\omega L_d} (0.0129(\pi/6 - (-\pi/6))) = \frac{3V_{LL}}{\pi\omega L_d} (0.0129 \frac{\pi}{3}) \\ I_d &= 0.0129 \frac{V_{LL}}{\omega L_d} \end{aligned}$$

Therefore,

$$L_{d,min} \simeq \frac{0.013}{\omega I_d} V_{LL}$$

# Problem 6-8

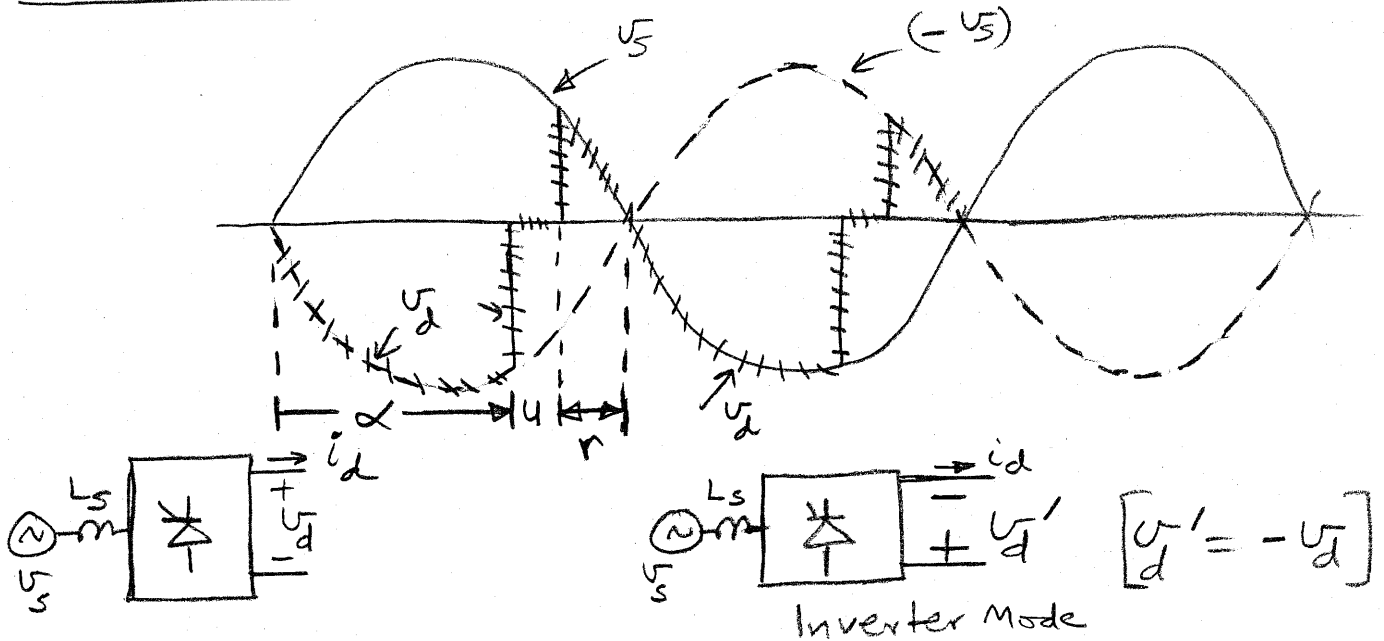

To represent the inverter mode of operation, often the output dc voltage polarity is defined as shown in the diagram to the right by  $v_d'$  where  $v_d' = -v_d$ .


If  $L_s = 0$  (and hence  $u = 0$ ) but  $r$  is the same as in the waveforms above, then we can calculate

$$V_d' (\text{with } L_s = 0) = 0.9 V_s \cos r$$

Because of a finite  $L_s$  and a finite  $u$ ,

$$V_d' = \overbrace{0.9 V_s \cos r}^{V_{d0}} - \frac{2\omega L_s}{\pi} I_d = V_{d0} \cos r - "R_u" I_d$$

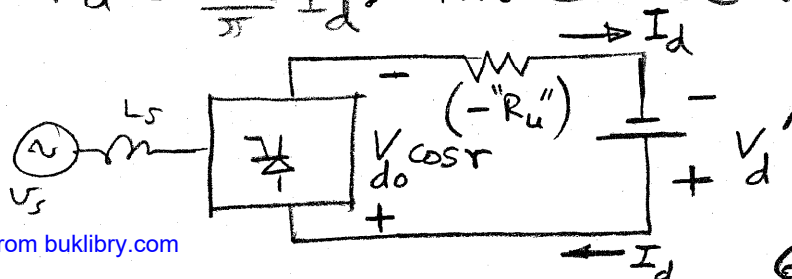where  $"R_u" = \frac{2\omega L_s}{\pi} I_d$ . This can be represented as below:



$$(b) \quad I_{\text{base}} = \frac{V_d/2}{Z_o} = \frac{77.5}{30.89} = 2.51 \text{ A}$$

From problem 9-1

$$I_{L,\text{peak}} = [1 + (V_o)N] \cdot I_{\text{base}} = (1 + 0.9) \cdot 2.51 = 4.77 \text{ A}$$

$$V_{C,\text{peak}} = 2V_{\text{base}} = 2 \cdot \frac{155}{2} = 155 \text{ V}$$

$$\therefore S = \left( \frac{1}{2} \cdot 22.12 \cdot 10^{-6} \cdot 4.77^2 \right) + \left( \frac{1}{2} \cdot 23.18 \cdot 10^{-9} \cdot 155^2 \right)$$

Download full file from [buklibry.com](https://buklibry.com)

$$= 10^{-6} \cdot (251.6 + 278.4) = 530.0 \mu\text{J}$$

# Problem 18-1

<https://buklibry.com/download/solutions-manual-of-power-electronics-converters-applications-and-design-by-mohan-undeland-2nd-edition/>

transformer: 240V, 25 kVA

$$\therefore \text{rated current} = \frac{25 \times 10^3}{240} = 104.17$$

$$\text{base impedance} = \frac{\text{rated voltage}}{\text{rated current}} = \frac{240}{104.17} = 2.3 \, \Omega$$

$$\text{and leakage impedance} = 0.04 \times \text{base impedance} = 0.092 \, \Omega$$

(a)

Therefore, the short-circuit current is

$$I_{sc} = \frac{240}{0.092} = 2604.2 \, \text{A}$$

and per-phase short-circuit capacity

$$\text{SCC} = \frac{240 \times 2604.2}{10^3} = 625 \, \text{kVA}$$

(b)

Load power is 5 kW at 240V and at <sup>a</sup>unity displacement power factor. Therefore, the fundamental current at full load is

$$I_1 = \frac{5 \times 10^3}{240} = 20.83 \, \text{A}$$

$$\frac{I_{sc}}{I_1} = \frac{2604.2}{20.83} = 125$$

$$\text{THD} = \sqrt{\sum_{h \neq 1} \left( \frac{I_h}{I_1} \right)^2} = 34.6\% \quad (\text{from Table P18-1})$$

Comparing THD and the harmonics of Table P18-1 with the limits in Table



Assume  $V_j = 0.8 \text{ V}$  ; Exact value not critical to an approximate estimate of  $I_{on,IGBT}$ .

$$I_{on,IGBT} = \frac{3! - 0.8}{R_{on,IGBT}} ; R_{on,IGBT} = \frac{W_d}{q(m_n + m_p)n_b A}$$

$$W_d = (10^{-5})(750) = 75 \text{ mm} ; R_{on,IGBT} = \frac{7.5 \times 10^{-3}}{(1.6 \times 10^{-19})(900)(10^{16})(2)} = 2.6 \times 10^{-3} \text{ W}$$

$$I_{on,IGBT} = \frac{2.2}{2.6 \times 10^{-3}} = 850 \text{ amps}$$

MOSFET current -  $I_{on,MOS}$  ;  $V_{on}(MOS) = I_{on,MOS} R_{on,MOS}$

$$I_{on,MOS} = \frac{V_{on}(MOS)}{R_{on,MOS}} ; R_{on,MOS} = \frac{W_d}{q m_n N_d A} ; W_d = 75 \text{ mm}$$

$$N_d = \frac{1.3 \times 10^{17}}{750} = 1.7 \times 10^{14} \text{ cm}^{-3}$$

$$R_{on,MOS} = \frac{7.5 \times 10^{-3}}{(1.6 \times 10^{-19})(1.5 \times 10^3)(1.7 \times 10^{14})(2)} = 0.09 \text{ ohms}$$

Download full file from [buklibry.com](https://buklibry.com)

$$I_{on,MOS} = \frac{3}{0.09} = 33 \text{ amps}$$