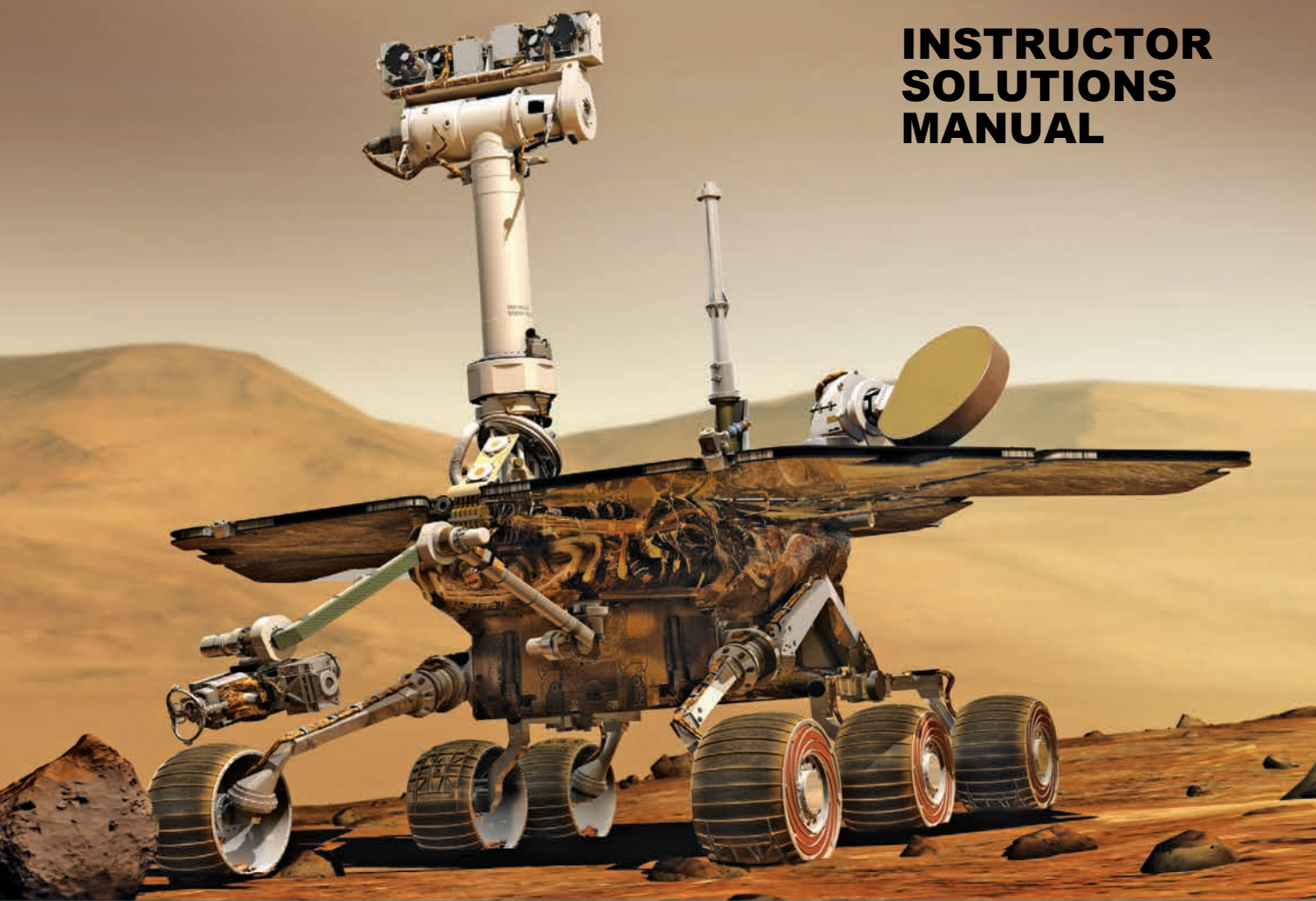


FIFTH EDITION

# Fundamentals of Electric Circuits

**INSTRUCTOR  
SOLUTIONS  
MANUAL**



Charles K. Alexander | Matthew N. O. Sadiku

### **Chapter 1, Solution 1**

(a)  $q = 6.482 \times 10^{17} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-103.84 \text{ mC}}$

(b)  $q = 1.24 \times 10^{18} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-198.65 \text{ mC}}$

(c)  $q = 2.46 \times 10^{19} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-3.941 \text{ C}}$

(d)  $q = 1.628 \times 10^{20} \times [-1.602 \times 10^{-19} \text{ C}] = \mathbf{-26.08 \text{ C}}$


## Chapter 1, Solution 2

- (a)  $i = dq/dt = 3 \text{ mA}$
- (b)  $i = dq/dt = (16t + 4) \text{ A}$
- (c)  $i = dq/dt = (-3e^{-t} + 10e^{-2t}) \text{ nA}$
- (d)  $i = dq/dt = 1200\pi \cos 120\pi t \text{ pA}$
- (e)  $i = dq/dt = -e^{-4t} (80 \cos 50t + 1000 \sin 50t) \mu\text{A}$

$$\begin{aligned}
 R_{eq} &= 4 + 1.829 + (3.977 + 7.368) \parallel (0.5964 + 14) \\
 &= 5.829 + 11.346 \parallel 14.5964 = \mathbf{12.21 \, \Omega} \\
 i &= 20 / (R_{eq}) = \mathbf{1.64 \, A}
 \end{aligned}$$

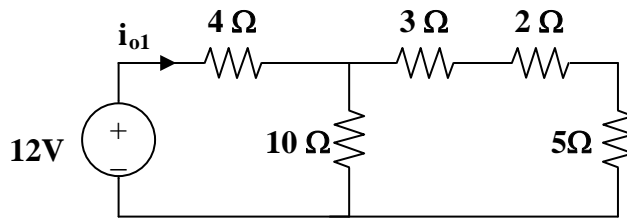
## Chapter 4, Solution 16.

Let  $i_o = i_{o1} + i_{o2} + i_{o3}$ , where  $i_{o1}$ ,  $i_{o2}$ , and  $i_{o3}$  are due to the 12-V, 4-A, and 2-A sources. For  $i_{o1}$ , consider the circuit below.



$$10 \parallel (3 + 2 + 5) = 5 \text{ ohms}, i_{o1} = 12/(5 + 4) = (12/9) \text{ A}$$

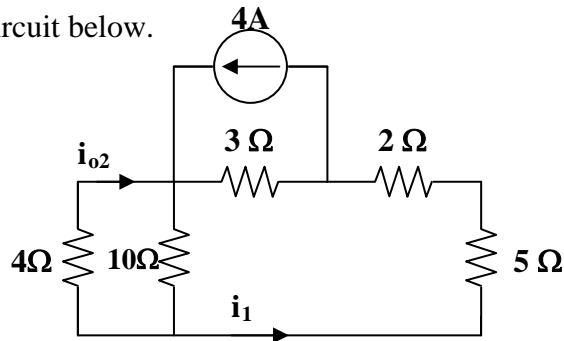
For  $i_{o2}$ , consider the circuit below.



$$2 + 5 + 4 \parallel 10 = 7 + 40/14 = 69/7$$

$$i_1 = [3/(3 + 69/7)]4 = 84/90, i_{o2} = [-10/(4 + 10)]i_1 = -6/9$$

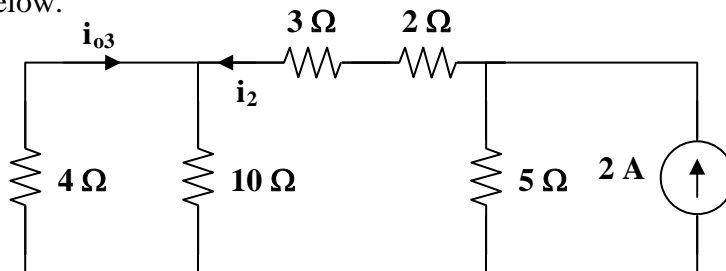For  $i_{o3}$ , consider the circuit below.



$$3 + 2 + 4 \parallel 10 = 5 + 20/7 = 55/7$$

$$i_2 = [5/(5 + 55/7)]2 = 7/9, i_{o3} = [-10/(10 + 4)]i_2 = -5/9$$

$$i_o = (12/9) - (6/9) - (5/9) = 1/9 = \mathbf{111.11 \text{ mA}}$$

$$(v_1 - 10\text{m})/(10\text{k}) + v_1/30\text{k} + (v_1 - 3.87\text{m})/20\text{k} = 0$$

or  $6v_1 - 60\text{m} + 2v_1 + 3v_1 - 11.61\text{m} = 0$

or  $v_1 = 71.61/11 = 6.51 \text{ mV}.$

The current through the 20k-ohm resistor, left to right, is,

$$i_{20} = (6.51\text{m} - 3.87\text{m})/20\text{k} = 132 \times 10^{-9} \text{ A}$$

thus,  $v_o = 3.87\text{m} - 132 \times 10^{-9} \times 80\text{k} = \mathbf{-6.69 \text{ mV}}.$

**Chapter 7, Solution 30.**

$$(a) \quad \int_{-\infty}^{\infty} 4t^2 \delta(t-1) dt = 4t^2 \Big|_{t=1} = \mathbf{4}$$

$$(b) \quad \int_{-\infty}^{\infty} 4t^2 \cos(2\pi t) \delta(t-0.5) dt = 4t^2 \cos(2\pi t) \Big|_{t=0.5} = \cos \pi = \mathbf{-1}$$

**Chapter 9, Solution 68.**

$$\mathbf{Y}_{\text{eq}} = \frac{1}{5 - j2} + \frac{1}{3 + j} + \frac{1}{-j4}$$


$$\mathbf{Y}_{\text{eq}} = (0.1724 + j0.069) + (0.3 - j0.1) + (j0.25)$$

$$\mathbf{Y}_{\text{eq}} = \mathbf{(472.4 + j219) \text{ mS}}$$



**Chapter 10, Solution 60.**

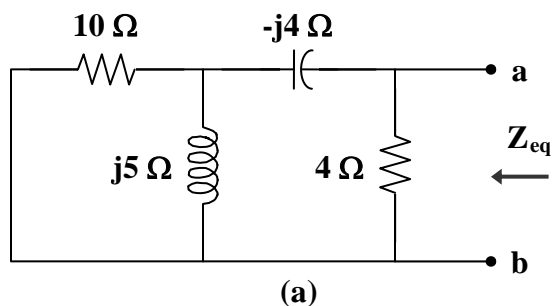- (a) To find  $\mathbf{Z}_{eq}$ , consider the circuit in Fig. (a).




$$\mathbf{Z}_{eq} = 4 \parallel (-j4 + 10 \parallel j5) = 4 \parallel (-j4 + 2 + j4)$$

$$\mathbf{Z}_{eq} = 4 \parallel 2$$

$$= 1.333 \, \Omega$$

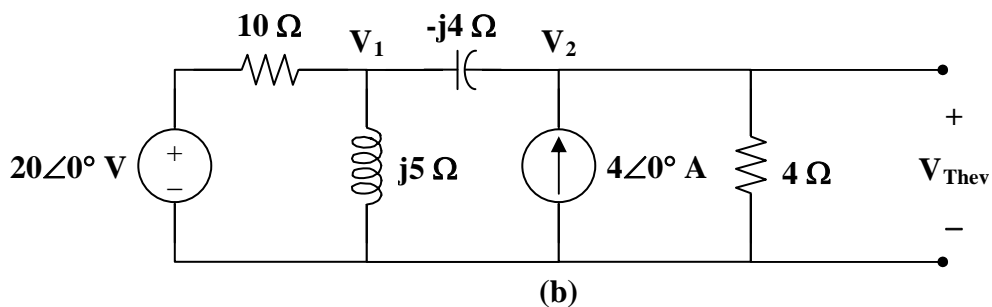- To find  $\mathbf{V}_{Thev}$ , consider the circuit in Fig. (b).



At node 1,

$$\begin{aligned} \frac{20 - \mathbf{V}_1}{10} &= \frac{\mathbf{V}_1}{j5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4} \\ (1 + j0.5) \mathbf{V}_1 - j2.5 \mathbf{V}_2 &= 20 \end{aligned} \quad (1)$$

At node 2,

$$\begin{aligned} 4 + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j4} &= \frac{\mathbf{V}_2}{4} \\ \mathbf{V}_1 &= (1 - j) \mathbf{V}_2 + j16 \end{aligned} \quad (2)$$

Substituting (2) into (1) leads to

$$\begin{aligned} 28 - j16 &= (1.5 - j3) \mathbf{V}_2 \\ \mathbf{V}_2 &= \frac{28 - j16}{1.5 - j3} = 8 + j5.333 \end{aligned}$$


**Chapter 11, Solution 34.**

$$\begin{aligned} f_{rms}^2 &= \frac{1}{T} \int_0^T f^2(t) dt = \frac{1}{3} \left[ \int_0^2 (3t)^2 dt + \int_2^3 6^2 dt \right] \\ &= \frac{1}{3} \left[ \frac{9t^3}{3} \Big|_0^2 + 36 \right] = 20 \\ f_{rms} &= \sqrt{20} = 4.472 \end{aligned}$$

$$f_{rms} = \mathbf{4.472}$$

# Chapter 19, Solution 5.

Consider the circuit in Fig. (a).

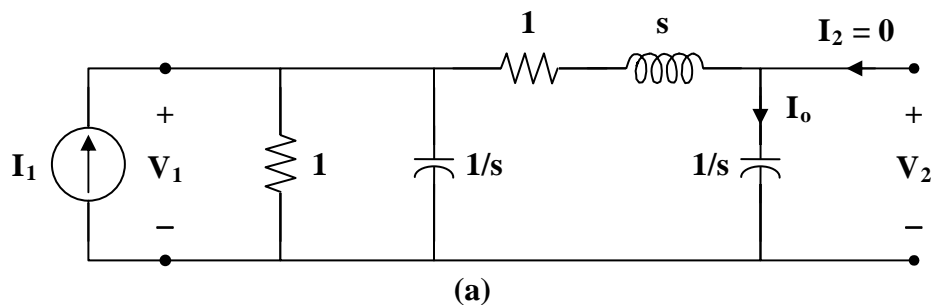

$$z_{11} = 1 \parallel \frac{1}{s} \parallel \left( 1 + s + \frac{1}{s} \right) = \frac{\frac{1}{s}}{1 + \frac{1}{s}} \parallel \left( 1 + s + \frac{1}{s} \right) = \frac{\left( \frac{1}{s+1} \right) \left( 1 + s + \frac{1}{s} \right)}{\left( \frac{1}{s+1} \right) + 1 + s + \frac{1}{s}}$$

$$z_{11} = \frac{s^2 + s + 1}{s^3 + 2s^2 + 3s + 1}$$

$$I_o = \frac{1 \parallel \frac{1}{s}}{1 \parallel \frac{1}{s} + 1 + s + \frac{1}{s}} I_1 = \frac{\frac{1}{s+1}}{\frac{1}{s+1} + 1 + s + \frac{1}{s}} I_1 = \frac{\frac{s}{s+1}}{\frac{s}{s+1} + s^2 + s + 1} I_1$$

$$I_o = \frac{s}{s^3 + 2s^2 + 3s + 1} I_1$$

$$V_2 = \frac{1}{s} I_o = \frac{I_1}{s^3 + 2s^2 + 3s + 1}$$

$$z_{21} = \frac{V_2}{I_1} = \frac{1}{s^3 + 2s^2 + 3s + 1}$$

Consider the circuit in Fig. (b).

