

DIGITAL DESIGN

With An Introduction to the Verilog HDL

FIFTH EDITION

M. MORRIS MANO | MICHAEL D. CILETTI



 


FIGURE 10.13

Graphic symbol for ripple counter, IC type 7493

the symbol $CT=0$. Since the count input does not go to the clock inputs of all flip-flops, it has no $C1$ label and, instead, the symbol $+$ is used to indicate a count-up operation. The dynamic symbol next to the $+$ together with the polarity symbol along the input line signify that the count is affected with a negative-edge transition of the input signal. The bit grouping from 0 to 2 in the output represents values for the weights to the power of 2. Thus, 0 represents the value of $2^0 = 1$ and 2 represents the value $2^2 = 4$.

The standard graphic symbol for the four-bit counter with parallel load, IC type 74161, is shown in Fig. 10.14. The qualifying symbol for a synchronous counter is CTR followed by the symbol $DIV16$ (divide by 16), which gives the cycle length of the counter. There is a single load input at pin 9 that is split into the two modes, $M1$ and $M2$. $M1$ is active when the load input at pin 9 is low and $M2$ is active when the load input at pin 9 is high. $M1$ is recognized as active low from the polarity indicator along its input line. The count-enable inputs use the G dependencies. $G3$ is associated with the T input and $G4$ with the P input of the count enable. The label associated with the clock is

$$C5/2, 3, 4 +$$

This means that the circuit counts up (the $+$ symbol) when $M2$, $G3$, and $G4$ are active (load = 1, $ENT = 1$, and $ENP = 1$) and the clock in $C5$ goes through a positive transition. This condition is specified in the function table of the 74161 listed in Fig. 9.15. The parallel inputs have the label 1, $5D$, meaning that the D inputs are active when $M1$ is active (load = 0) and the clock goes through a positive transition. The output carry is designated by the label

$$3CT = 15$$

This is interpreted to mean that the output carry is active (equal to 1) if $G3$ is active ($ENT = 1$) and the content (CT) of the counter is 15 (binary 1111). Note that the outputs

- 7.7** (a) 7×128 decoders, 256 AND gates (b) $x = 46; y = 112$
7.8 (a) 8 chips (b) 18; 15 (c) 3×8 decoder
7.10 0001 1011 1011 1
7.11 101 110 011 001 010
7.12 (a) 0101 1010; (b) 1100 0110; (c) 1111 0100
7.13 (a) 6 (b) 7 (c) 7
7.14 (a) 0101010
7.16 24 pins
7.20 Product terms: $yz', xz', x'y'z, xy', x'y, z$
7.25 $A = yz' + xz' + x'y'z$
 $B = x'y' + yz + y'z'$
 $C = A + xyz$
 $D = z + x'y$

CHAPTER 8

- 8.1** (a) The transfer and increment occur concurrently, i.e., at the same clock edge. After the transfer, $R2$ holds the contents that were in $R1$ before the clock edge, and $R2$ holds its previous value incremented by 1.
 (b) Decrement the content of $R3$ by one.
 (c) If ($S_1 = 1$), transfer content of $R1$ to $R0$. If ($S_1 = 0$ and $S_2 = 1$), transfer content of $R2$ to $R0$.
8.7 RTL notation:
 $S0$: Initial state: if (start = 1) then ($RA \leftarrow \text{data_A}, RB \leftarrow \text{data_B}$, go to $S1$).
 $S1$: { Carry, RA } $\leftarrow RA + (2\text{'s complement of } RB)$, go to $S2$.
 $S2$: If (borrow = 0) go to $S0$. If (borrow = 1) then $RA \leftarrow (2\text{'s complement of } RA)$, go to $S0$.